



Звіт

З лабораторної роботи №3

З дисципліни: «Моделювання комп'ютерних систем»

На тему: «Поведінковий опис цифрового автомата Перевірка роботи автомата за допомогою стенда Elbert V2 – Spartan3A FPGA»

Варіант 23

Виконав

Студент групи КІ-201

Равчак В.А.

Перевірив:

Козак Н.Б.

Мета роботи: На базі стенда Elbert V2 – Spartan3A FPGA реалізувати цифровий автомат для обчислення значення виразу дотримуючись наступних вимог

Мій варіант - №23

| ВАРІАНТ(КІ-201) | ВИРАЗ |
|-----------------|--------------------------------|
| 23 | $((OP1 - 2) + OP2 + 10) \gg 1$ |

Рис. 1 - скріншот заданого варіанту

Виконання роботи

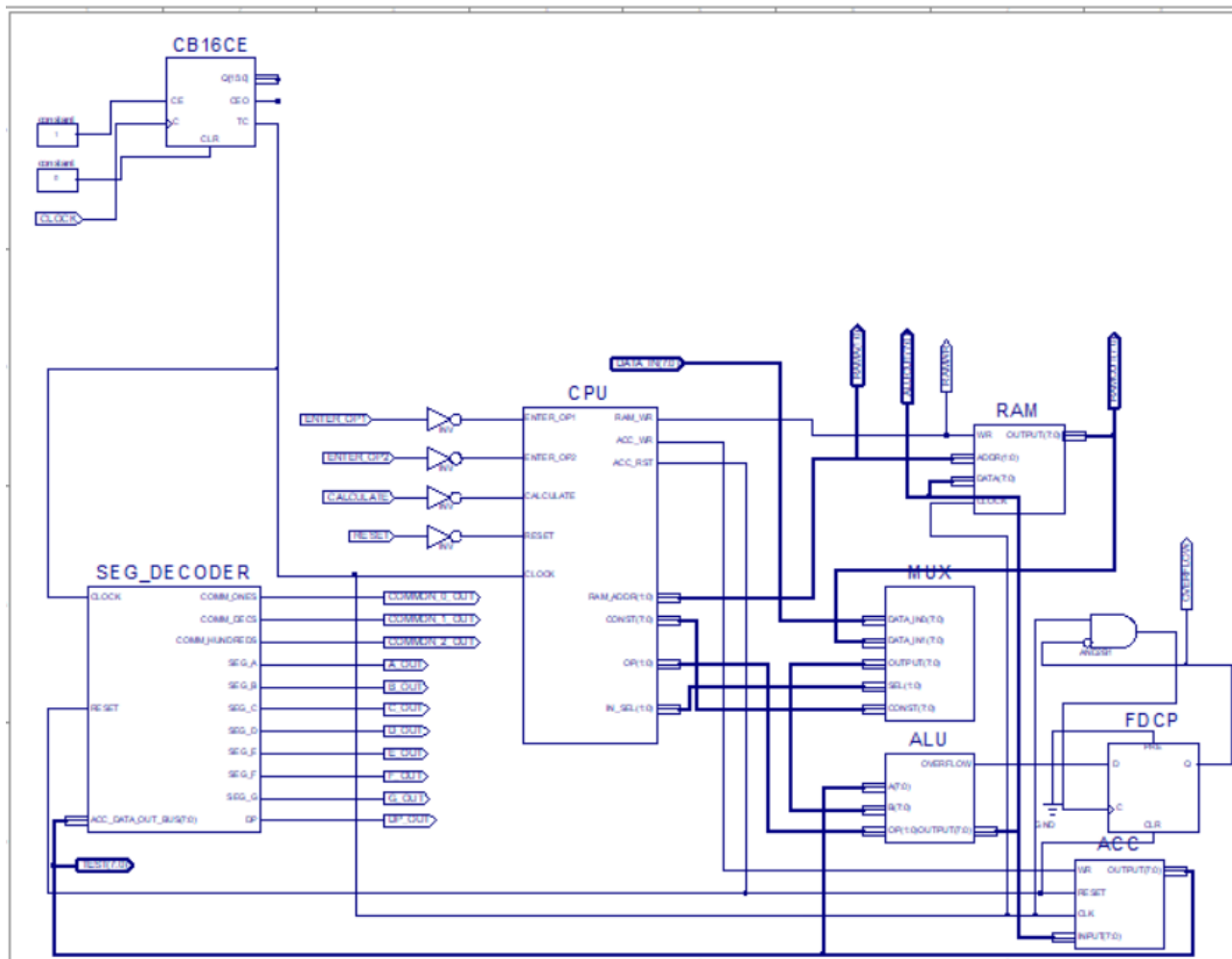


Рис. 2 - Top Level

Файл ACC.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ACC is
    Port ( WR : in STD_LOGIC;
          RESET : in STD_LOGIC;
          CLK : in STD_LOGIC;
```

```

        INPUT : in STD_LOGIC_VECTOR (7 downto 0);
        OUTPUT : out STD_LOGIC_VECTOR (7 downto 0));
end ACC;

architecture ACC_arch of ACC is
    signal DATA : STD_LOGIC_VECTOR (7 downto 0);
begin
    process (CLK)
    begin
        if rising_edge(CLK) then
            if RESET = '1' then
                DATA <= (others => '0');
            elsif WR = '1' then
                DATA <= INPUT;
            end if;
        end if;
    end process;

    OUTPUT <= DATA;

end ACC_arch;

```

Файл ALU.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ALU is
    Port ( A : in STD_LOGIC_VECTOR(7 downto 0);
          B : in STD_LOGIC_VECTOR(7 downto 0);
          OP : in STD_LOGIC_VECTOR(1 downto 0);
          OUTPUT : out STD_LOGIC_VECTOR(7 downto 0);
          OVERFLOW: out STD_LOGIC);
end ALU;

```

architecture ALU_Behavioral of ALU is

```
    signal ALUR: STD_LOGIC_VECTOR(15 downto 0) := (others => '0');
```

```
    signal Carry: STD_LOGIC := '0';
```

```
begin
```

```
    process(A, B, OP)
```

```
    begin
```

```
        case (OP) is
```

```
            when "01" => ALUR <= ("00000000" & A) + ("00000000" & B);
```

```
            when "10" => ALUR <= ("00000000" & A) + ("11111111" & not B) + "0000000000000001";
```

```
            when "11" => ALUR <= std_logic_vector(unsigned(("00000000" & A)) srl to_integer(unsigned(B)));  
            ALUR(15 downto 8) <= "00000000";
```

```
            when others => ALUR <= ("00000000" & B);
```

```
        end case;
```

```
    end process;
```

```
    OUTPUT <= ALUR(7 downto 0);
```

```
    OVERFLOW <= ALUR(8) OR ALUR(9) OR ALUR(10) OR ALUR(11) OR  
    ALUR(12) OR ALUR(13) OR ALUR(14) OR ALUR(15);
```

```
end ALU_Behavioral;
```

Файл CPU.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity CPU is
```

```
    port( ENTER_OP1 : IN STD_LOGIC;
```

```
          ENTER_OP2 : IN STD_LOGIC;
```

```
          CALCULATE : IN STD_LOGIC;
```

```
          RESET : IN STD_LOGIC;
```

```
          CLOCK : IN STD_LOGIC;
```

```
          RAM_WR : OUT STD_LOGIC;
```

```
          RAM_ADDR : OUT STD_LOGIC_VECTOR(1 DOWNT0 0);
```

```
          CONST : OUT STD_LOGIC_VECTOR(7 DOWNT0 0);
```

```
          ACC_WR : OUT STD_LOGIC;
```

```
          ACC_RST : OUT STD_LOGIC;
```

```
          IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
```

```
          OP : OUT STD_LOGIC_VECTOR(1 DOWNT0 0));
```

```
end CPU;
```

architecture CPU_arch of CPU is

```
type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2, RUN_CALC0,  
RUN_CALC1, RUN_CALC2, RUN_CALC3, RUN_CALC4, FINISH);
```

```
signal CUR_STATE : STATE_TYPE;
```

```
signal NEXT_STATE : STATE_TYPE;
```

```
begin
```

```
    SYNC_PROC: process (CLOCK)
```

```
    begin
```

```
        if (rising_edge(CLOCK)) then
```

```
            if (RESET = '1') then
```

```
                CUR_STATE <= RST;
```

```
            else
```

```
                CUR_STATE <= NEXT_STATE;
```

```
            end if;
```

```
        end if;
```

```
    end process;
```

```
    NEXT_STATE_DECODE: process (CLOCK, ENTER_OP1, ENTER_OP2,  
CALCULATE)
```

```
    begin
```

```
        NEXT_STATE <= CUR_STATE;
```

```
        case(CUR_STATE) is
```

```
            when RST =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when IDLE =>
```

```
                if (ENTER_OP1 = '1') then
```

```
                    NEXT_STATE <= LOAD_OP1;
```

```
                elsif (ENTER_OP2 = '1') then
```

```
                    NEXT_STATE <= LOAD_OP2;
```

```
                elsif (CALCULATE = '1') then
```

```
                    NEXT_STATE <= RUN_CALC0;
```

```
                else
```

```
                    NEXT_STATE <= IDLE;
```

```
                end if;
```

```
            when LOAD_OP1 =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when LOAD_OP2 =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when RUN_CALC0 =>
```

```

        NEXT_STATE <= RUN_CALC1;
    when RUN_CALC1 =>
        NEXT_STATE <= RUN_CALC2;
    when RUN_CALC2 =>
        NEXT_STATE <= RUN_CALC3;
    when RUN_CALC3 =>
        NEXT_STATE <= RUN_CALC4;
    when RUN_CALC4 =>
        NEXT_STATE <= FINISH;
    when FINISH      =>
        NEXT_STATE <= FINISH;
    when others      =>
        NEXT_STATE <= IDLE;
end case;
end process;

```

```

OUTPUT_DECODE: process (CUR_STATE)
begin

```

```

    case (CUR_STATE) is
        when RST =>
            RAM_WR <= '0';
            RAM_ADDR <= "00";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when LOAD_OP1 =>
            RAM_WR <= '1';
            RAM_ADDR <= "00";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when LOAD_OP2 =>
            RAM_WR <= '1';
            RAM_ADDR <= "01";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when RUN_CALC0 =>

```

```

        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '1';
        ACC_RST <= '0';
        IN_SEL <= "01";
        OP <= "01";
    when RUN_CALC1 =>
        RAM_WR <= '0';
        RAM_ADDR <= "01";
        CONST <= "00000010";
        ACC_WR <= '1';
        ACC_RST <= '0';
        IN_SEL <= "10";
        OP <= "10";
    when RUN_CALC2 =>
        RAM_WR <= '0';
        RAM_ADDR <= "01";
        CONST <= "00000000";
        ACC_WR <= '1';
        ACC_RST <= '0';
        IN_SEL <= "01";
        OP <= "01";
    when RUN_CALC3 =>
        RAM_WR <= '0';
        RAM_ADDR <= "01";
        CONST <= "00001010";
        ACC_WR <= '1';
        ACC_RST <= '0';
        IN_SEL <= "10";
        OP <= "01";
    when RUN_CALC4 =>
        RAM_WR <= '0';
        RAM_ADDR <= "01";
        CONST <= "00000001";
        ACC_WR <= '1';
        ACC_RST <= '0';
        IN_SEL <= "10";
        OP <= "11";
    when IDLE =>
        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '0';

```

```

        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";
    when others =>
        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";
    end case;
end process;
end CPU_arch;

```

Файл MUX.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX is
    PORT(
        SEL: in STD_LOGIC_VECTOR(1 downto 0);
        CONST: in STD_LOGIC_VECTOR(7 downto 0);
        --CONST1: in STD_LOGIC_VECTOR()
        DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);
        DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);
        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)
    );
end MUX;

architecture Behavioral of MUX is
begin
    process (SEL, DATA_IN0, DATA_IN1, CONST)
    begin
        if (SEL = "00") then
            OUTPUT <= DATA_IN0;
        elsif (SEL = "01") then
            OUTPUT <= DATA_IN1;
        else
            OUTPUT <= CONST;
        end if;
    end process;
end Behavioral;

```


Файл RAM.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity RAM is
    port(
        WR : IN STD_LOGIC;
        ADDR : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        DATA : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        CLOCK: IN STD_LOGIC;
        OUTPUT : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
end RAM;

architecture RAM_arch of RAM is
    type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
    signal UNIT : ram_type;

begin
    process(ADDR, CLOCK, UNIT)
    begin
        if(rising_edge(CLOCK)) then
            if (WR = '1') then
                UNIT(conv_integer(ADDR)) <= DATA;
            end if;
        end if;
        OUTPUT <= UNIT(conv_integer(ADDR));
    end process;
end RAM_arch;
```

Файл SEG_DECODER.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```

entity SEG_DECODER is
    port( CLOCK : IN STD_LOGIC;
          RESET : IN STD_LOGIC;
          ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7
DOWNTO 0);
          COMM_ONES          : OUT STD_LOGIC;
          COMM_DECS          : OUT STD_LOGIC;
          COMM_HUNDREDS      : OUT STD_LOGIC;
          SEG_A              : OUT STD_LOGIC;
          SEG_B              : OUT STD_LOGIC;
          SEG_C              : OUT STD_LOGIC;
          SEG_D              : OUT STD_LOGIC;
          SEG_E              : OUT STD_LOGIC;
          SEG_F              : OUT STD_LOGIC;
          SEG_G              : OUT STD_LOGIC;
          DP                 : OUT STD_LOGIC);
end SEG_DECODER;

architecture Behavioral of SEG_DECODER is

    signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
    signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
    signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";

begin
    BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
        variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
        variable bcd      : STD_LOGIC_VECTOR(11 downto 0) ;
    begin
        bcd      := (others => '0') ;
        hex_src  := ACC_DATA_OUT_BUS;

        for i in hex_src'range loop
            if bcd(3 downto 0) > "0100" then
                bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
            end if ;
            if bcd(7 downto 4) > "0100" then
                bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
            end if ;
            if bcd(11 downto 8) > "0100" then
                bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
            end if ;
        end loop
    end process
end Behavioral

```

```

        bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new
entry
        hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; -- shift
src + pad with 0
    end loop ;

```

```

HONDREDS_BUS    <= bcd (11 downto 8);
DECS_BUS        <= bcd (7 downto 4);
ONES_BUS        <= bcd (3 downto 0);

```

```

end process BIN_TO_BCD;

```

```

INDICATE : process(CLOCK)
    type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

    variable CUR_DIGIT    : DIGIT_TYPE := ONES;
    variable DIGIT_VAL     : STD_LOGIC_VECTOR(3 downto 0) :=
"0000";
    variable DIGIT_CTRL    : STD_LOGIC_VECTOR(6 downto 0) :=
"0000000";
    variable COMMONS_CTRL : STD_LOGIC_VECTOR(2 downto 0) :=
"000";

```

```

    begin

```

```

        if (rising_edge(CLOCK)) then

```

```

            if(RESET = '0') then

```

```

                case CUR_DIGIT is

```

```

                    when ONES =>

```

```

                        DIGIT_VAL := ONES_BUS;

```

```

                        CUR_DIGIT := DECS;

```

```

                        COMMONS_CTRL := "001";

```

```

                    when DECS =>

```

```

                        DIGIT_VAL := DECS_BUS;

```

```

                        CUR_DIGIT := HUNDREDS;

```

```

                        COMMONS_CTRL := "010";

```

```

                    when HUNDREDS =>

```

```

                        DIGIT_VAL := HONDREDS_BUS;

```

```

                        CUR_DIGIT := ONES;

```

```

                        COMMONS_CTRL := "100";

```

```

                    when others =>

```

```

                        DIGIT_VAL := ONES_BUS;

```

```

                        CUR_DIGIT := ONES;

```

```

                        COMMONS_CTRL := "000";

```

```

                end case;

```

```

case DIGIT_VAL is      --abcdefg
    when "0000" => DIGIT_CTRL :=
"1111110";
    when "0001" => DIGIT_CTRL :=
"0110000";
    when "0010" => DIGIT_CTRL :=
"1101101";
    when "0011" => DIGIT_CTRL :=
"1111001";
    when "0100" => DIGIT_CTRL :=
"0110011";
    when "0101" => DIGIT_CTRL :=
"1011011";
    when "0110" => DIGIT_CTRL :=
"1011111";
    when "0111" => DIGIT_CTRL :=
"1110000";
    when "1000" => DIGIT_CTRL :=
"1111111";
    when "1001" => DIGIT_CTRL :=
"1111011";
    when others => DIGIT_CTRL :=
"0000000";

end case;
else
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := ONES;
    COMMONS_CTRL := "000";
end if;

COMM_ONES      <= not COMMONS_CTRL(0);
COMM_DECS      <= not COMMONS_CTRL(1);
COMM_HUNDREDS <= not COMMONS_CTRL(2);

SEG_A <= not DIGIT_CTRL(6);
SEG_B <= not DIGIT_CTRL(5);
SEG_C <= not DIGIT_CTRL(4);
SEG_D <= not DIGIT_CTRL(3);
SEG_E <= not DIGIT_CTRL(2);
SEG_F <= not DIGIT_CTRL(1);
SEG_G <= not DIGIT_CTRL(0);
DP    <= '1';

```

```

end if;
end process INDICATE;

end Behavioral;

```

 


Рис. 3 – Часова діаграма ACC

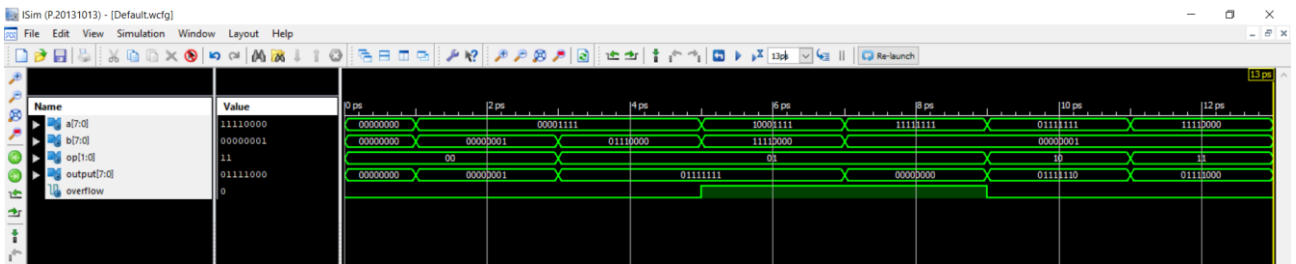


Рис. 4 – Часова діаграма ALU

 


Рис. 5 – Часова діаграма MUX

 


Рис. 6 – Часова діаграма RAM



Рис 7. – Часова діграма SEG_DECODER

 


Рис 8. – Часова діаграма TopLevel

Файл TopLevelTest.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY TopLevel_TopLevel_sch_tb IS
END TopLevel_TopLevel_sch_tb;
ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS

    COMPONENT TopLevel
    PORT( CLOCK      :    IN    STD_LOGIC;
          RESET      :    IN    STD_LOGIC;
          ENTER_OP1  :    IN    STD_LOGIC;
          ENTER_OP2  :    IN    STD_LOGIC;
          CALCULATE   :    IN    STD_LOGIC;
          DATA_IN    :    IN    STD_LOGIC_VECTOR (7 DOWNTO 0);
          COMMON_0_OUT :    OUT   STD_LOGIC;
          COMMON_1_OUT :    OUT   STD_LOGIC;
          COMMON_2_OUT :    OUT   STD_LOGIC;
          TEST: OUT STD_LOGIC_VECTOR(7 downto 0);

          A_OUT       :    OUT   STD_LOGIC;
          B_OUT       :    OUT   STD_LOGIC;
          C_OUT       :    OUT   STD_LOGIC;
          D_OUT       :    OUT   STD_LOGIC;
          E_OUT:      OUT   STD_LOGIC;
          F_OUT:      OUT   STD_LOGIC;
          G_OUT       :    OUT   STD_LOGIC;
          DP_OUT      :    OUT   STD_LOGIC;
          RAMOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
    
```

```

        ALUOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
        RAMA: OUT STD_LOGIC_VECTOR(1 downto 0);
        RAMWR: OUT STD_LOGIC;
    OVERFLOW :    OUT STD_LOGIC);
END COMPONENT;

SIGNAL CLOCK    :    STD_LOGIC := '0';
SIGNAL RESET    :    STD_LOGIC;
SIGNAL ENTER_OP1 :    STD_LOGIC;
SIGNAL ENTER_OP2 :    STD_LOGIC;
SIGNAL CALCULATE :    STD_LOGIC;
SIGNAL DATA_IN:    STD_LOGIC_VECTOR (7 DOWNT0 0);
SIGNAL COMMON_0_OUT :    STD_LOGIC;
SIGNAL COMMON_1_OUT :    STD_LOGIC;
SIGNAL COMMON_2_OUT :    STD_LOGIC;
SIGNAL A_OUT    :    STD_LOGIC;
SIGNAL B_OUT    :    STD_LOGIC;
SIGNAL C_OUT    :    STD_LOGIC;
SIGNAL D_OUT    :    STD_LOGIC;
SIGNAL E_OUT    :    STD_LOGIC;
SIGNAL F_OUT    :    STD_LOGIC;
SIGNAL G_OUT    :    STD_LOGIC;
SIGNAL DP_OUT   :    STD_LOGIC;
SIGNAL OVERFLOW :    STD_LOGIC;
    SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);
    SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal ALUOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMA: STD_LOGIC_VECTOR(1 downto 0);
    signal RAMWR: STD_LOGIC;

--    constant CLOCK_period : time := 166ns;
--    constant CLKP: time := 12ms;--24ms;

BEGIN

    UUT: TopLevel PORT MAP(
        CLOCK => CLOCK,
        RESET => RESET,
        ENTER_OP1 => ENTER_OP1,
        ENTER_OP2 => ENTER_OP2,
        CALCULATE => CALCULATE,
        DATA_IN => DATA_IN,
        COMMON_0_OUT => COMMON_0_OUT,

```

```

COMMON_1_OUT => COMMON_1_OUT,
COMMON_2_OUT => COMMON_2_OUT,
A_OUT => A_OUT,
B_OUT => B_OUT,
C_OUT => C_OUT,
D_OUT => D_OUT,
E_OUT => E_OUT,
F_OUT => F_OUT,
G_OUT => G_OUT,
DP_OUT => DP_OUT,
OVERFLOW => OVERFLOW,
TEST => TEST,
RAMOUT => RAMOUT,
ALUOUT => ALUOUT,
RAMA => RAMA,
RAMWR => RAMWR
);

CLOCK_process: process
begin
    CLOCK <= '0';
    wait for 83ns;
    CLOCK <= '1';
    wait for 83ns;
end process;

-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    lp1: for i in 6 to 6 loop
        lp2: for j in 2 to 2 loop
            TEST2 <= std_logic_vector(to_unsigned(i - 2 + j + 10,
8) srl 1);

            ENTER_OP1 <= '1';
            ENTER_OP2 <= '1';
            CALCULATE <= '1';
            DATA_IN <= (others => '0');
            RESET <= '0';
            wait for CLKP;
            RESET <= '1';
            wait for CLKP;
            DATA_IN <= std_logic_vector(to_unsigned(i, 8)); -- A
            ENTER_OP1 <= '0';
            wait for CLKP;

```



```

ENTER_OP1 <= '1';
wait for CLKP;
DATA_IN <= std_logic_vector(to_unsigned(j, 8)); -- B
ENTER_OP2 <= '0';
wait for CLKP;
ENTER_OP2 <= '1';
wait for CLKP;
CALCULATE <= '0'; -- START CALCULATION
wait for CLKP* 7;
assert TEST = TEST2 severity FAILURE;
wait for CLKP;

    end loop;
end loop;

    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***

END;

```

 


Рис.9 – 7-сегментний індикатор

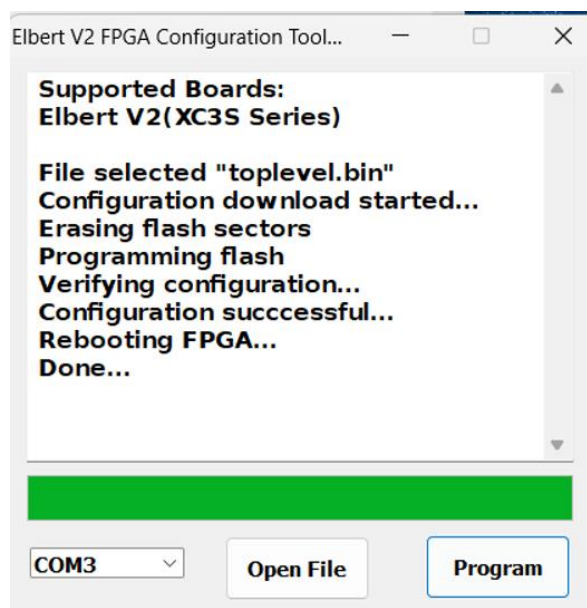


Рис.10 – Успішне прошиття плати

Висновок: Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.